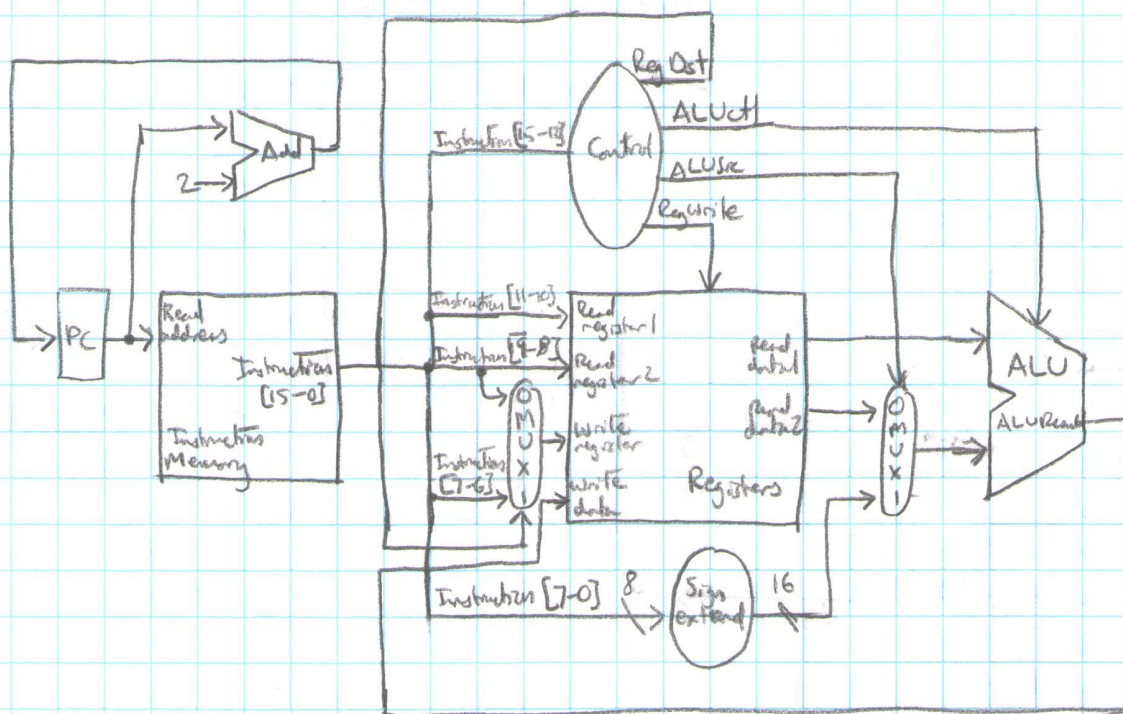


Overview: Simplified cycle datapath for R-type & addi instructions (16-bit MIPS)



Reg Array Implementation:

- PC
- Instruction memory

Behavioral:

- Main Control
- Register File
- Sign-Extend/Adder

Gate-Level:

- ALU
- Multiplexers

→ Logic diagrams only for ALU & multiplexers are shown, not for HA/FA.

Instruction Set Architecture/Control Unit Truth Table:

Instr	Opcode	Reg Dst	ALUSrc	RegWrite	ALUOp
add	0000	1	0	1	0010
sub	0001	1	0	1	0110
and	0010	1	0	1	0000
or	0011	1	0	1	0001
nor	0100	1	0	1	1100
nand	0101	1	0	1	1101
slt	0110	1	0	1	0111
addi	0111	0	1	1	0010

Input → Opcode  
Output → ALUOp

R-type: add, sub, and, or, nor, nand, slt  
I-type: addi

Instruction Formats:

R-format (add, sub, and, or, nor, nand, slt)

op	rs	rt	rd	unused
4	2	2	2	6


I-type (addi)

op	rs	rt	addr/value
4	2	2	8



\*No Zero or Overflow\*


## 16-bit ALU:

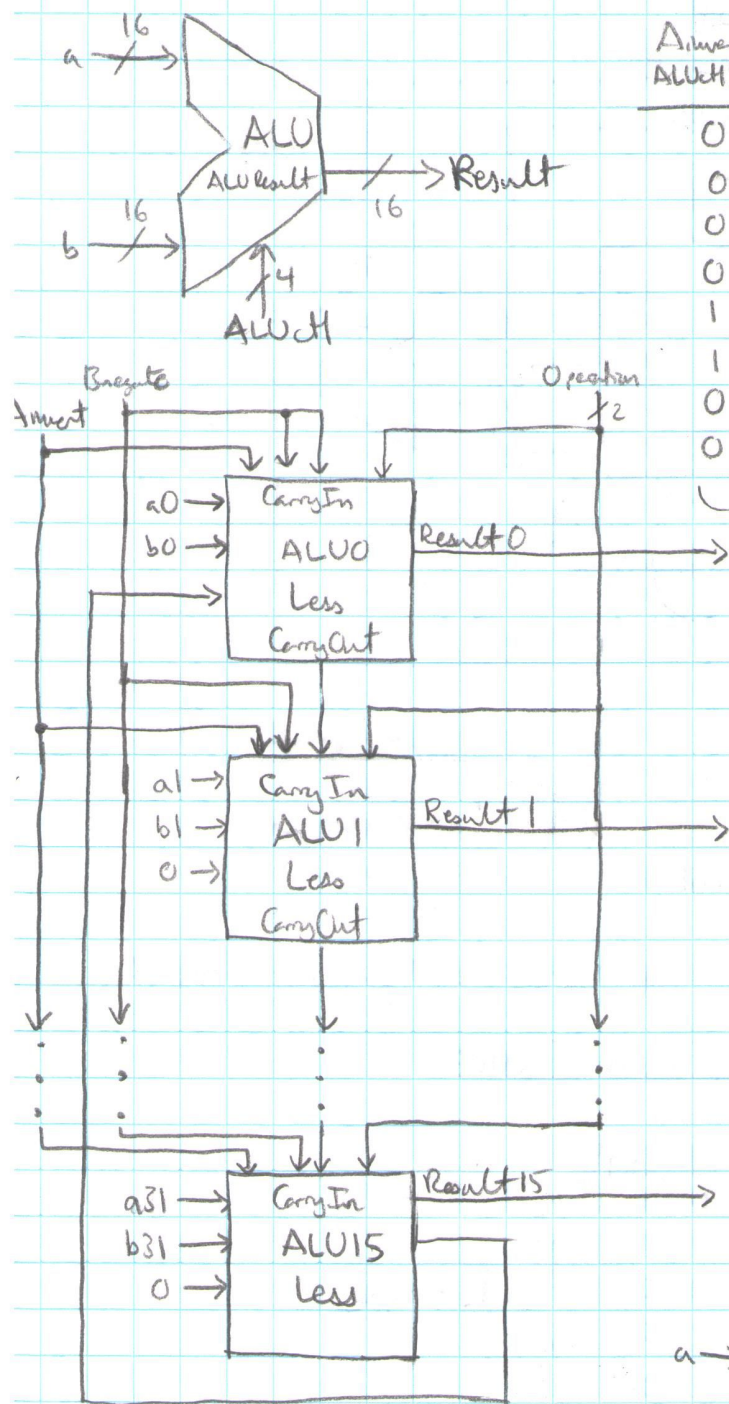


## ALU Control Lines:

Argument ALU[15:8]	Argument ALU[7:0]	Operation ALU[15:0]	Instr.
0	0	10	add
0	1	10	sub
0	0	00	and
0	0	01	or
1	1	00	xor
1	1	01	nand
0	1	11	slt
0	0	10	addi



## ALU0 to ALU14: 1-bit ALU, cascaded.

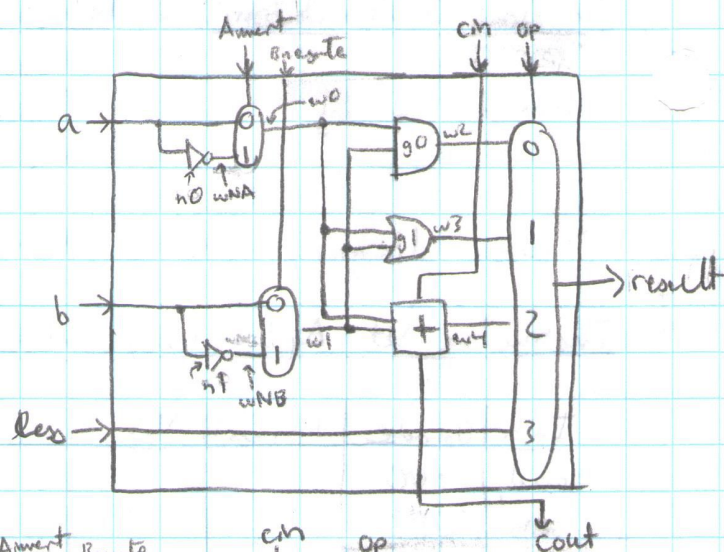


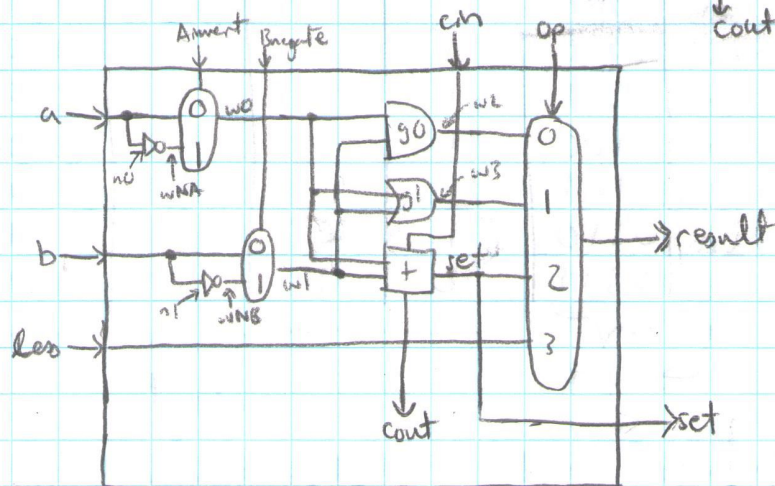
ALU 15: 1-bit ALU,  
last of the  
cascaded  
chain of ALU's.  
Slightly different





### 1-bit 2x1 Multiplexer:

  
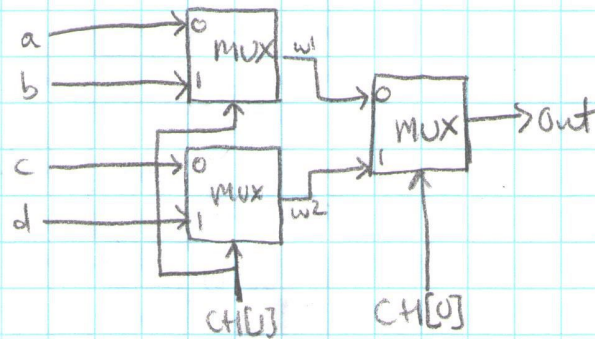 
### 1-bit 4x1 Multiplexer: Implemented by cascading 2x1 multiplexers.


  
### 2-bit 2x1 Multiplexer: Multiplexes 2 inputs of 2-bit data





16-bit 2x1 multiplexer: Multiplexes 2 inputs of 16-bit data.

\* Implemented by cascading 8 2x1 multiplexers for 2-bits, as shown below.\*

